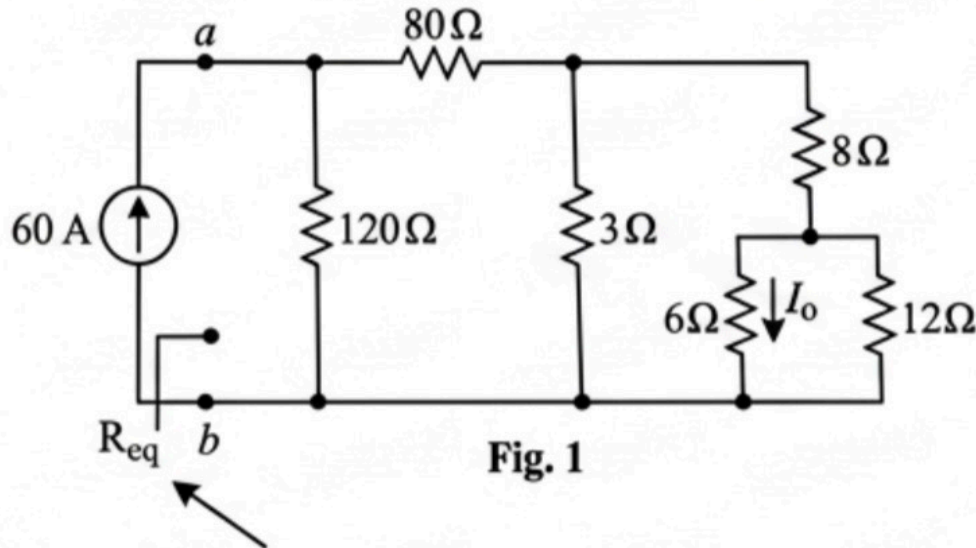


**Electrical circuits 1, Mid Term Exam, Summer semester, 2021-2022,
Date: 7-8-2022, Exam Time: 50 minutes**

Choose the correct answer

For the questions 1,2,3 consider the circuit shown in figure 1 and answer:



1. Current source is:
a. 20 A
b. 80 A
c. 60 A
2. Current values is:
a. 3 A
b. 120 A
c. 120 A
3. Current values is:
a. 80 A
b. 80 A
c. 120 A

For the questions 4,5,6,7,8 consider the circuit shown in figure 2 and answer:

4. Current values is:
a. 10 A
b. 4 A
c. 3 A

5. Current values is:
a. 13 A
b. 20 A
c. 4 A

6. Current values is:
a. 13 A
b. 5 A
c. 10 A

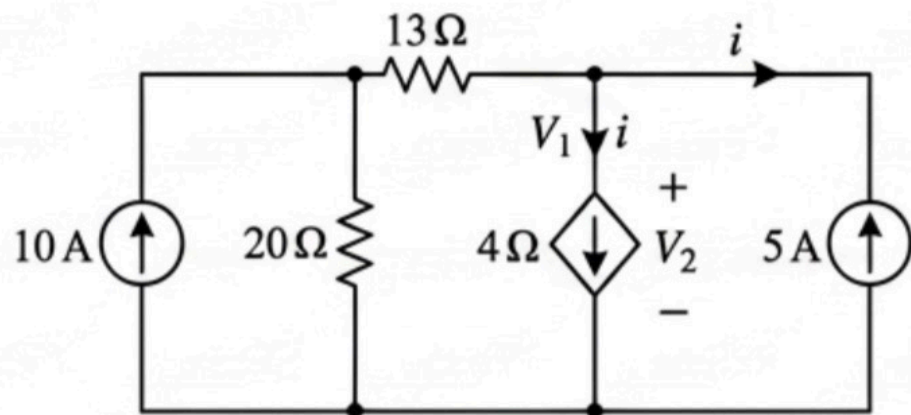


Fig. 2



Questions continued...

7. The current current of the volume value is:

- a. $8\ \Omega$ b. $120\ \Omega$ c. $30\ \Omega$ d. $3\ \Omega$

8. The value of the equivalent resistance is:

- a. $6\ \Omega$ b. $6\ \Omega$ c. $12\ \Omega$ d. $3\ \Omega$

For the questions 9,10,11 consider the circuit shown in figure 3 and answer:

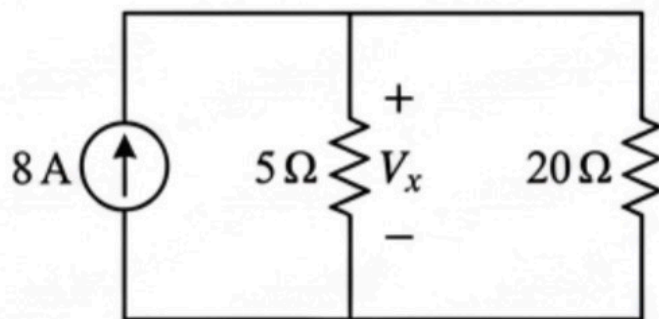


Fig. 3

9. The loot current current is:

- a. $8\ \Omega$ b. $20\ \Omega$

10. The loot current correent is:

- a. $5\ \Omega$ b. $20\ \Omega$
c. $3\ \Omega$ d. $20\ \Omega$

11. The loot current current is:

- a. $5\ \Omega$ b. $20\ \Omega$
c. $5\ \Omega$ d. $41\ \Omega$

12. Refer to figure 4; the value of the equivalent resistance is:

- a. $25\ \Omega$
b. $30\ \Omega$
c. $5\ \Omega$
d. $15\ \Omega$

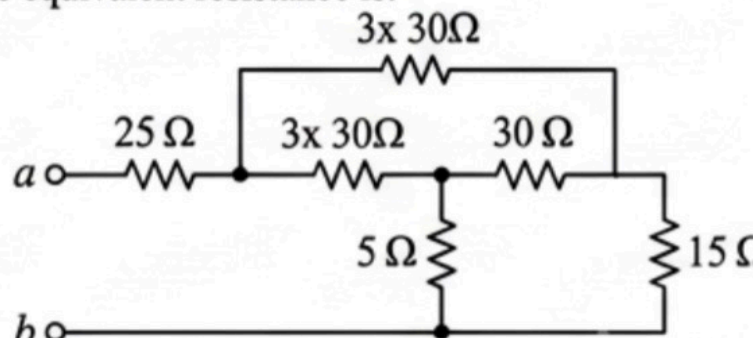


Fig. 4

13. Questions text; the resistance is:

- a. $25\ \Omega$ b. $30\ \Omega$ c. $50\ \Omega$

14. Questions text; the value of the equivalent source is:

- a. $15\ \Omega$ b. $5\ \Omega$ c. $20\ \Omega$ d. $25\ \Omega$

15. Questions text; the value of the equivalent source is:

- a. $5\ \Omega$ b. $2.5\ \Omega$ c. $30\ \Omega$ d. $12\ \Omega$