

Refer to approximate output waveform in fig. 1, select the correct circuit arrangement in fig.2 that will give this approximate output waveform?



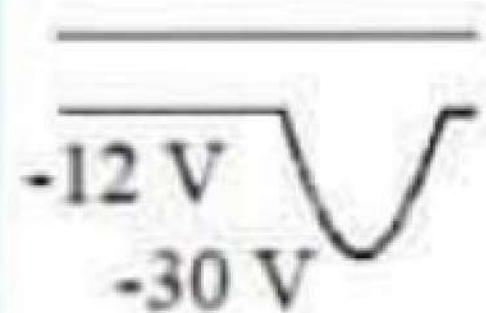



Fig. 1

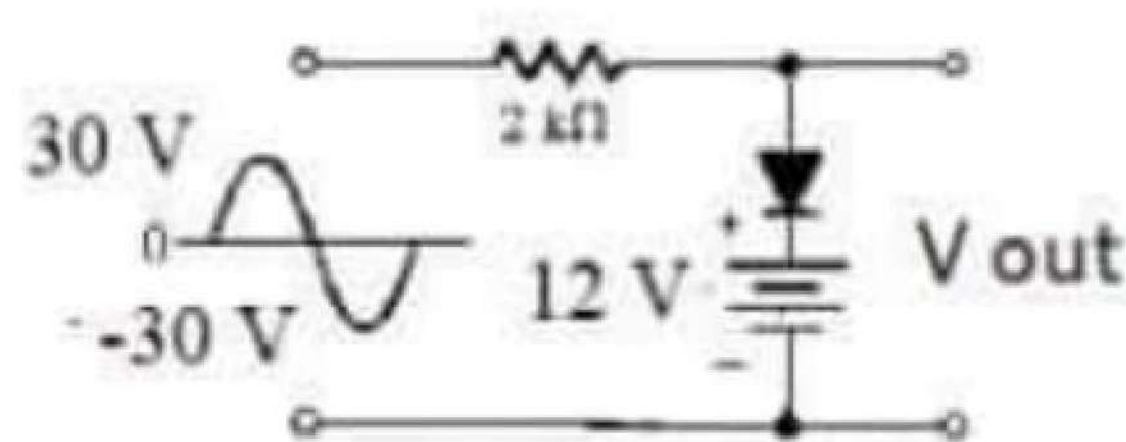


(a)

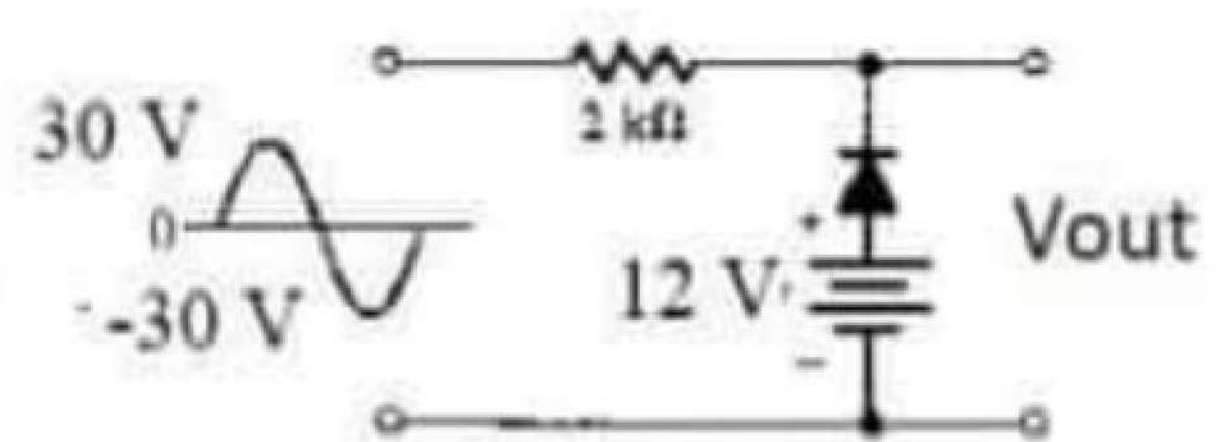

(b)

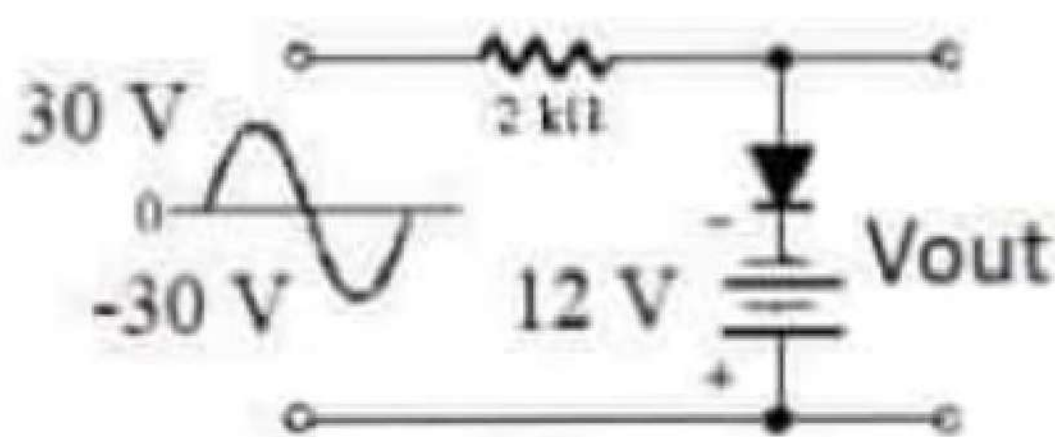

(c)

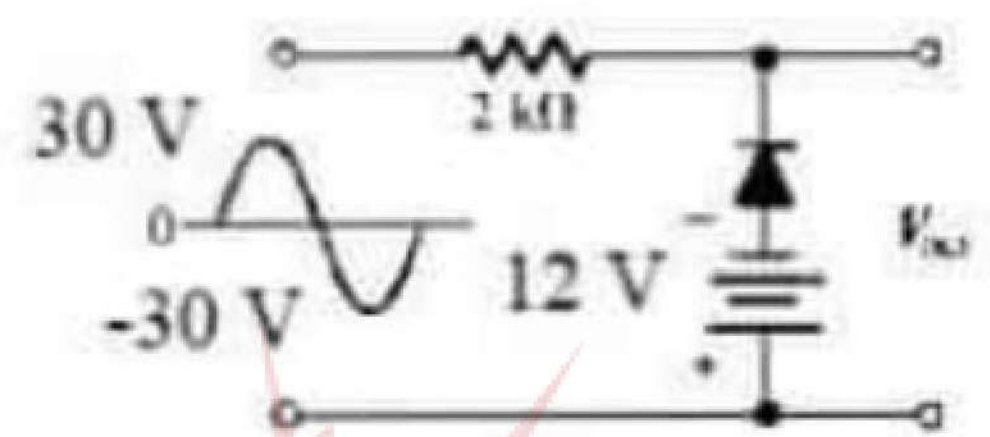

(d)

Fig. 2

Select one:

a. a

b. b

c. c

d. d

Refer to approximate output waveform waveform in fig. 1, select the correct circuit arrangement in fig.2 that will give this approximate output waveform?

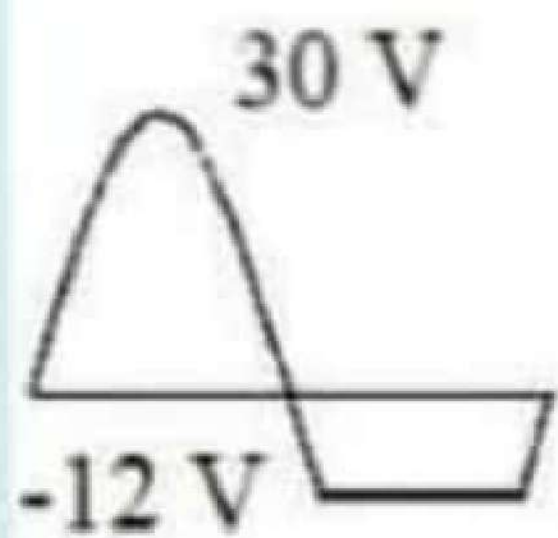


Fig. 1

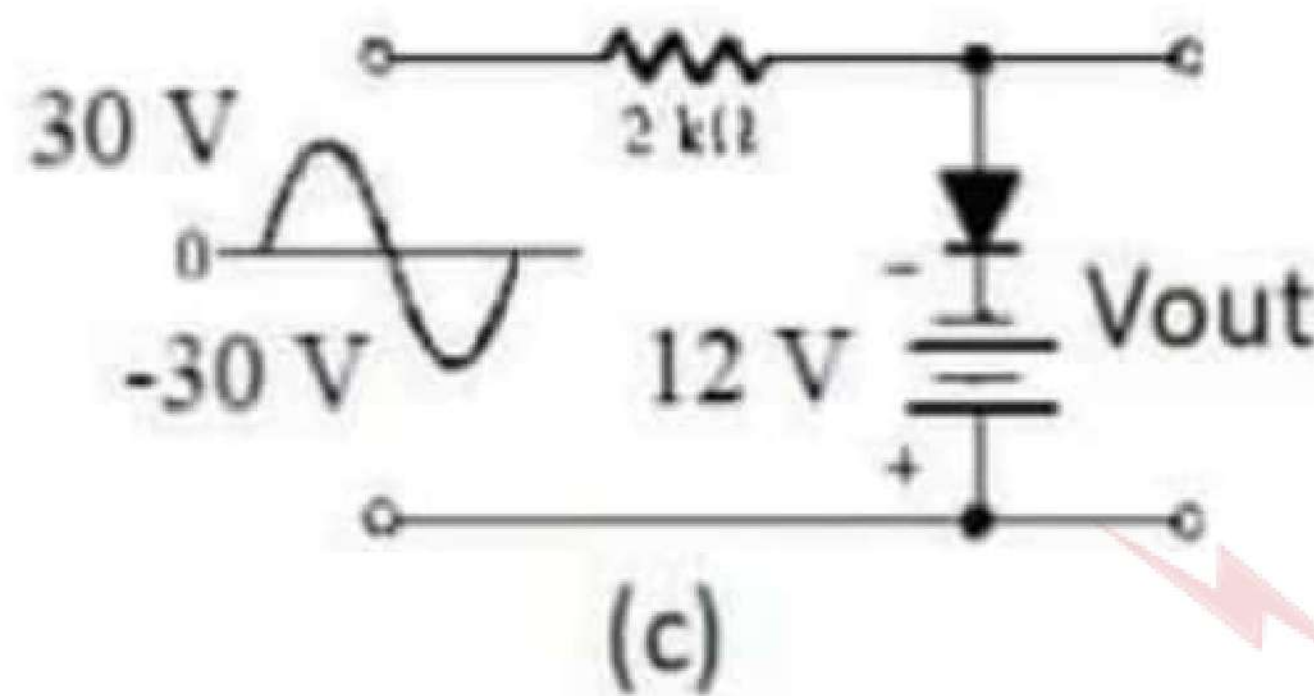
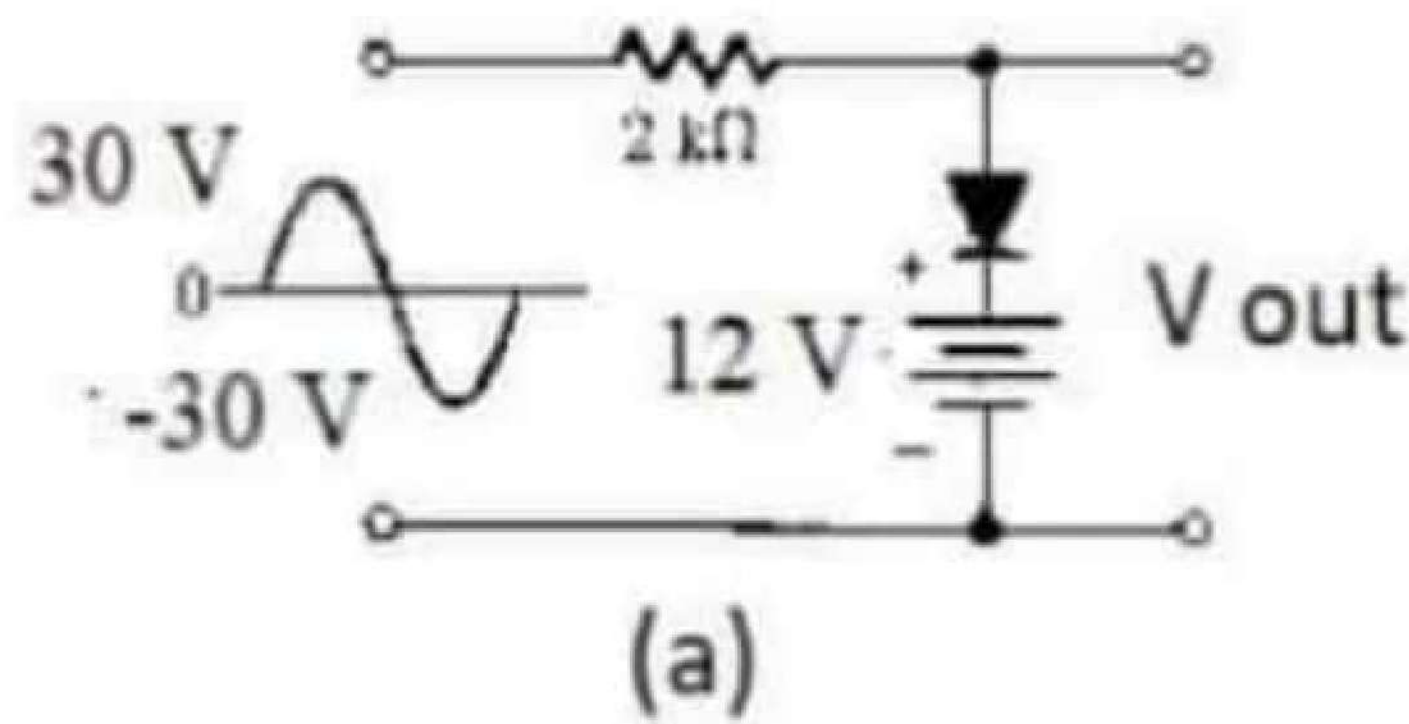


Fig. 2

Select one:

- ☐ a. a
- ☐ b. b
- ☐ c. c
- ☐ d. d

Refer to approximate output waveform waveform in fig. 1, select the correct circuit arrangement in fig.2 that will give this approximate output waveform?

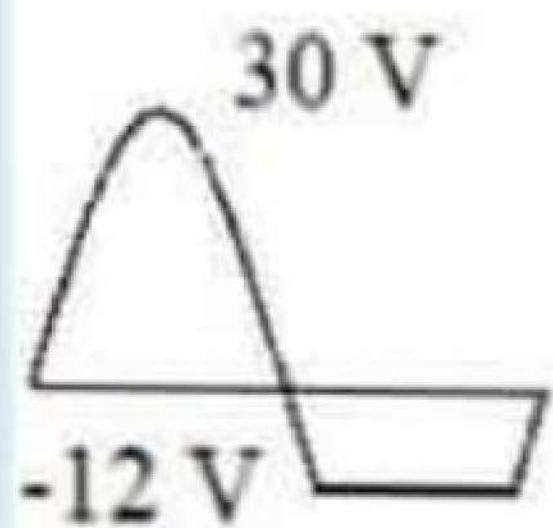


Fig. 1

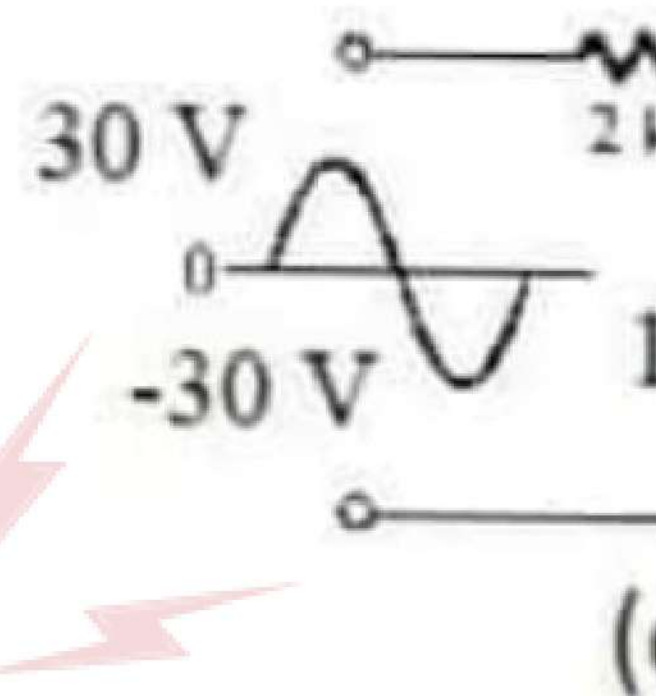
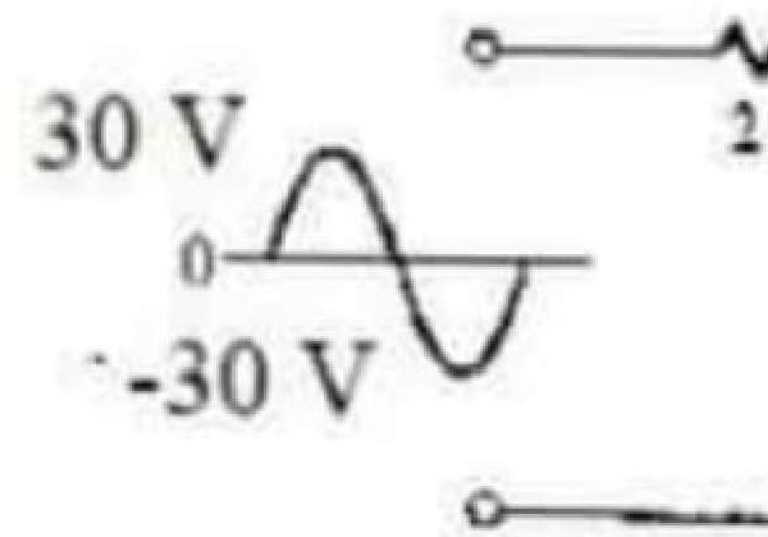
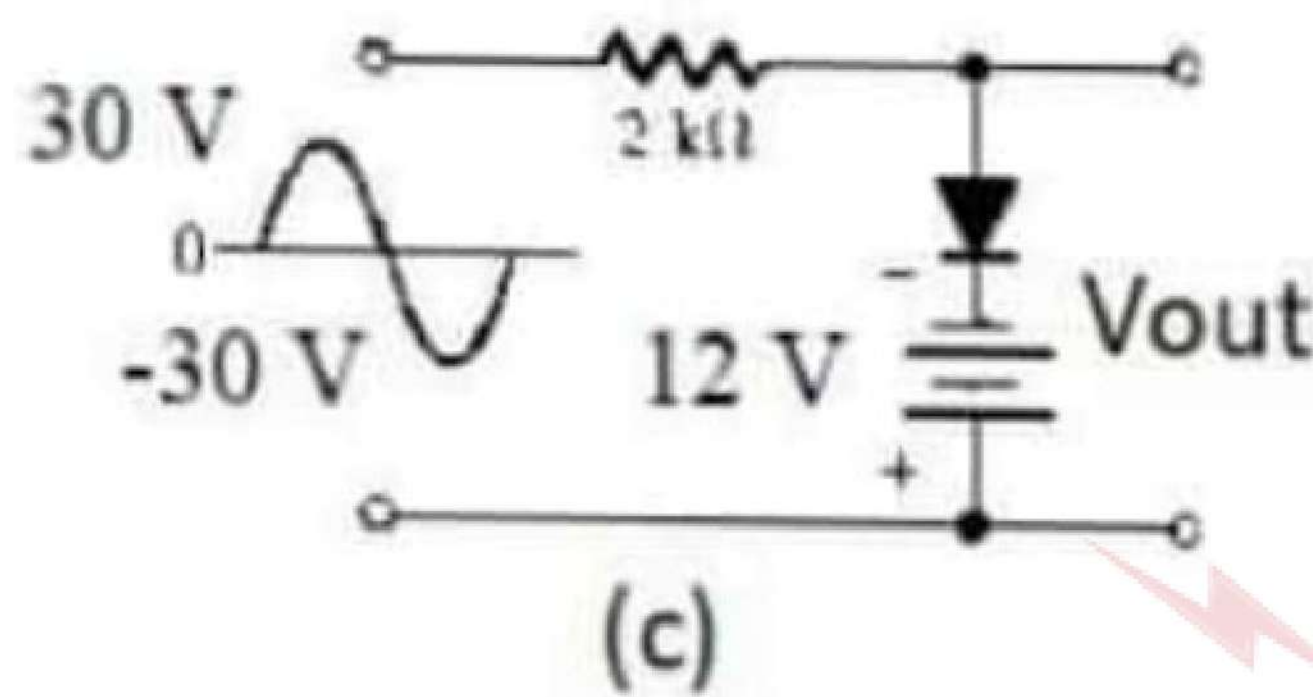
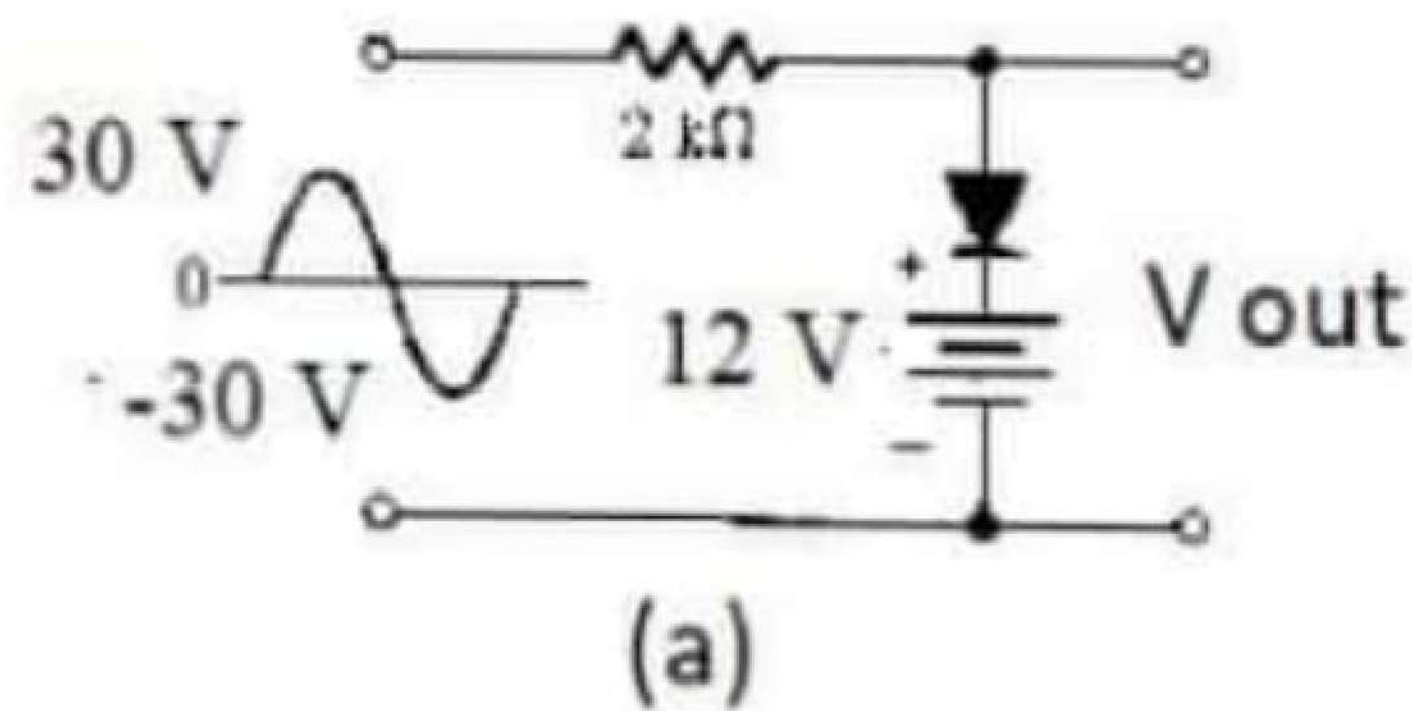


Fig. 2

Select one:


a. a

b. b

c. c

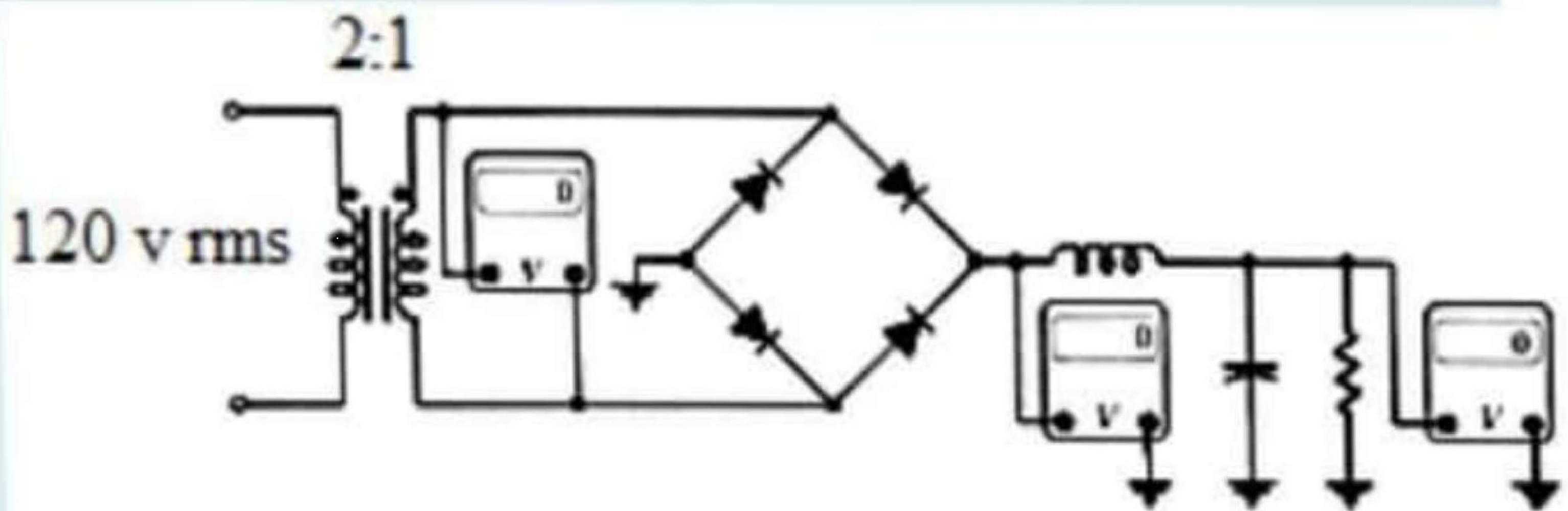d. d





Refer to Figure shown. If the voltmeter across the transformer reads 0 V, the probable trouble, if any, would be



Select one:

- ☐ a. an open transformer secondary.
- ☐ b. one of the diodes is open.
- ☐ c. the filter capacitor is shorted.
- ☐ d. no trouble exists.
- ☐ e. a diode is shorted.

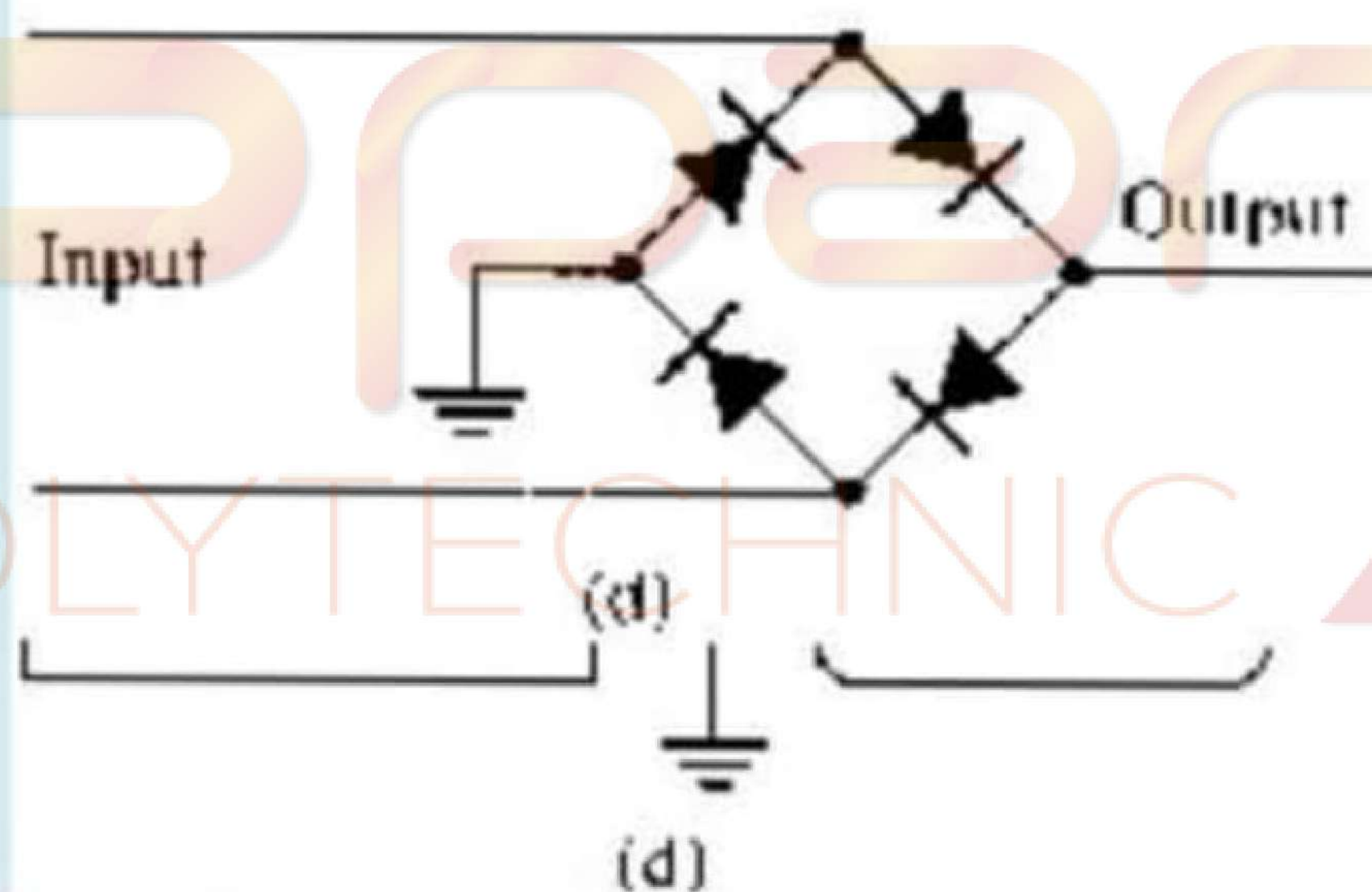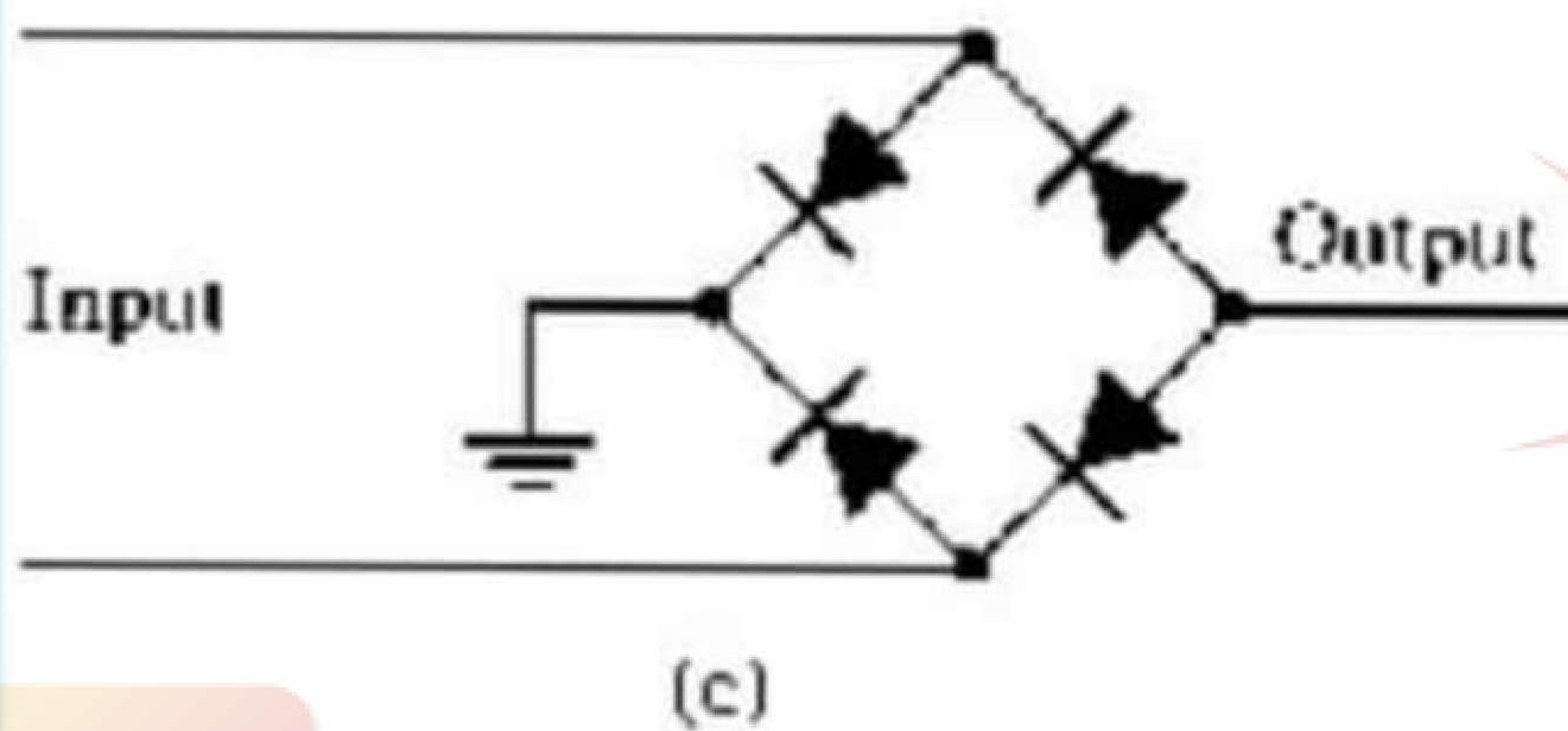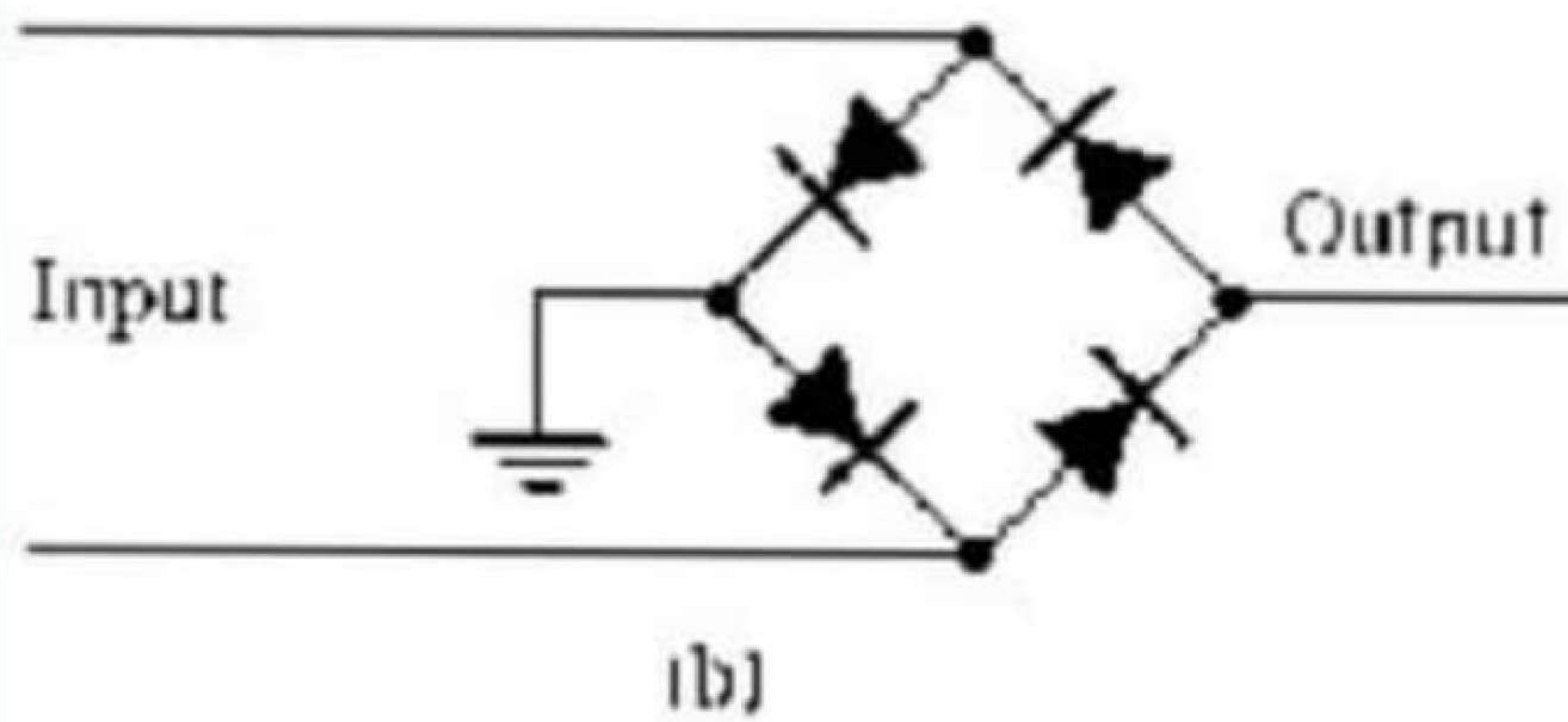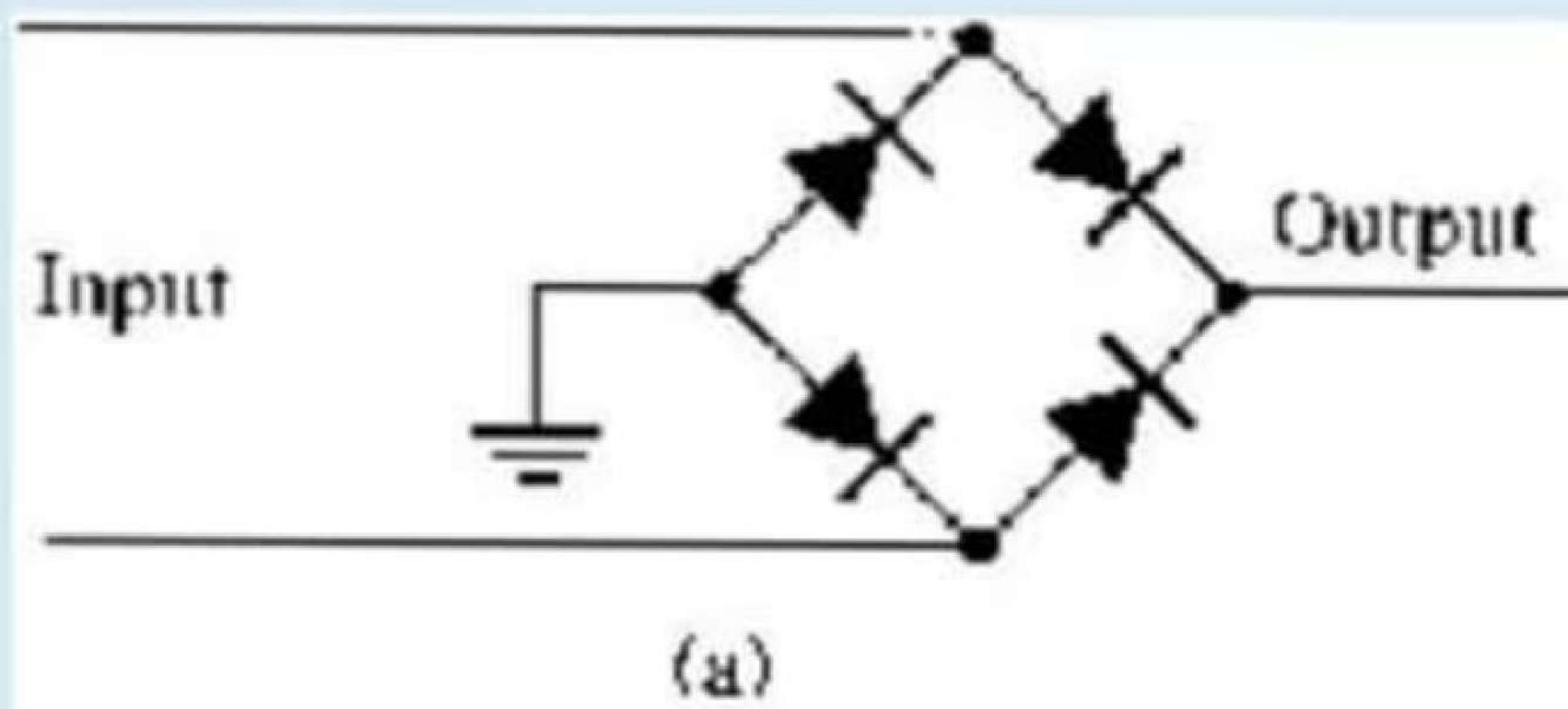Refer to Figure shown. Which diode arrangement will supply a positive output voltage?



In the operation of a half-wave rectifier with a capacitor-input filter, the ripple factor can be lowered by _____ the value of the filter capacitor or _____ the load resistors.

Select one:


- ☐ a. decreasing, increasing
- ☐ b. decreasing, decreasing
- ☐ c. increasing, increasing
- ☐ d. increasing, decreasing

A diode conducts current when reverse-biased and blocks current when forward-biased

Select one:

☐ a. True

☐ b. False

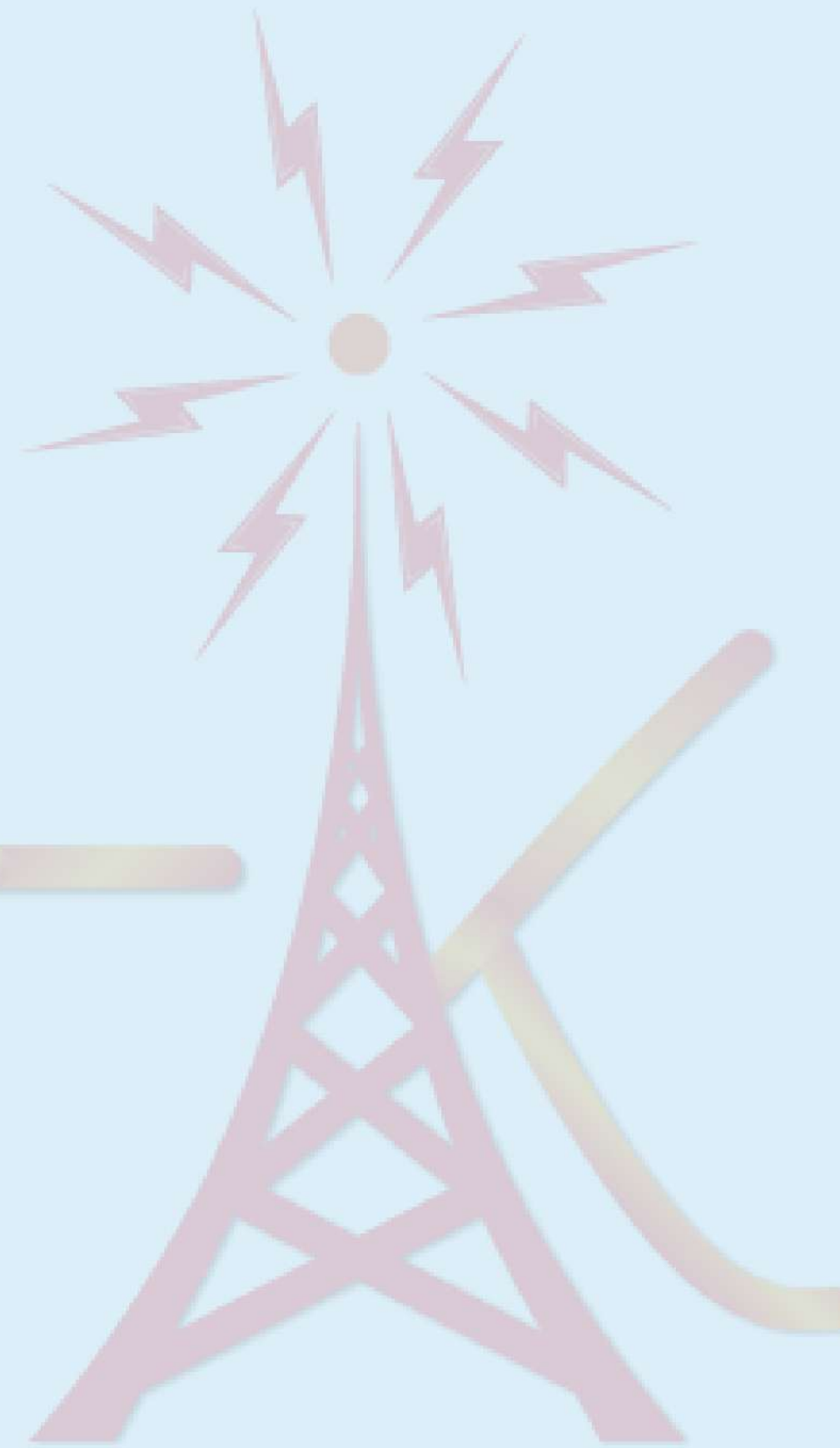

The diode characteristic curve is a plot between


Select one:

- ☐ a. current and time
- ☐ b. voltage and temprature
- ☐ c. voltage and time
- ☐ d. voltage and current

Actual resistance of a forward biased diode is typically much less than

Select one:

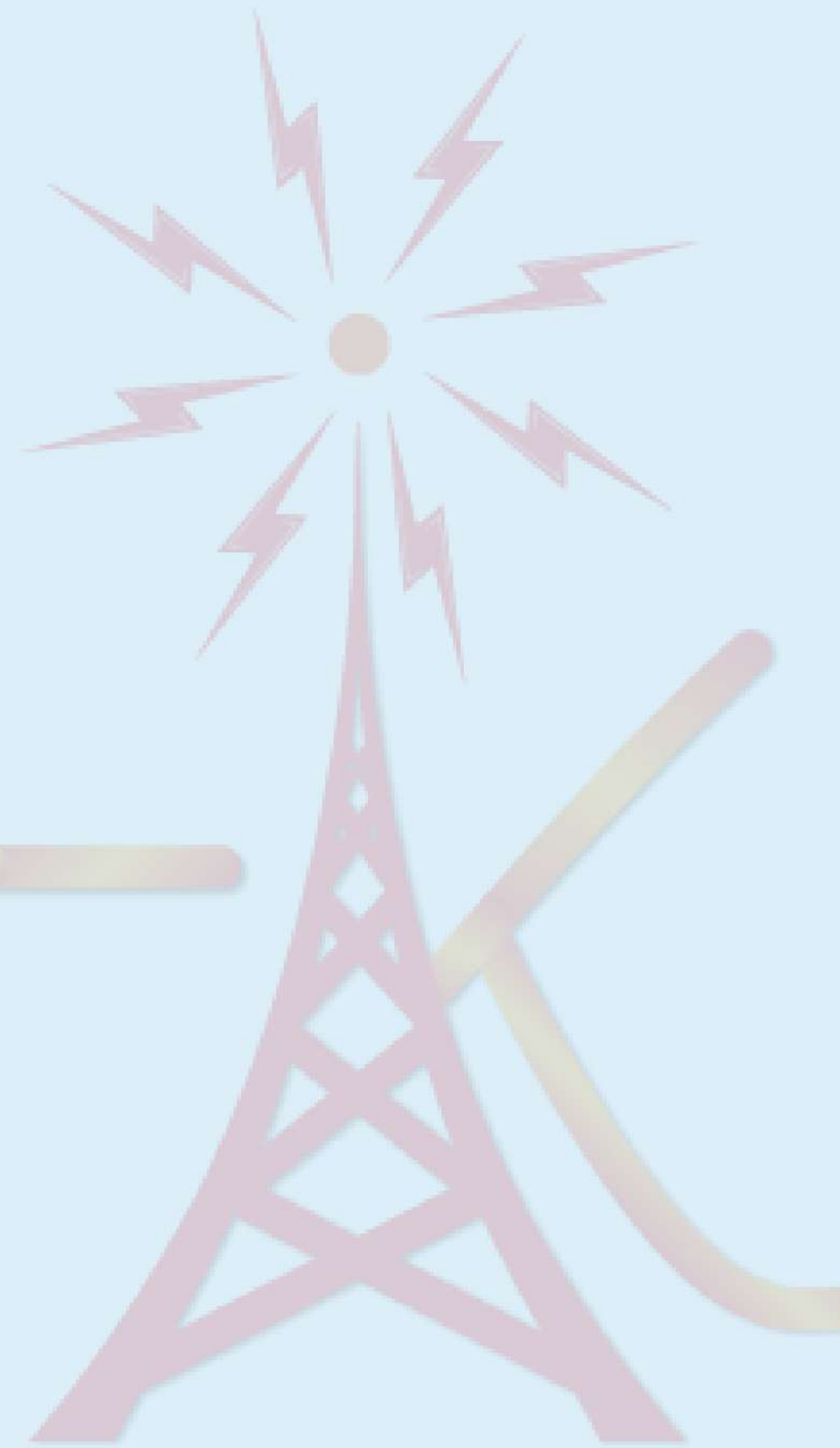
- ☐ a. $100\ \Omega$
- ☐ b. $500\ \Omega$
- ☐ c. $100\text{k}\ \Omega$
- ☐ d. $500\ \text{k}\Omega$



Condition in which diode never intentionally operate is

Select one:

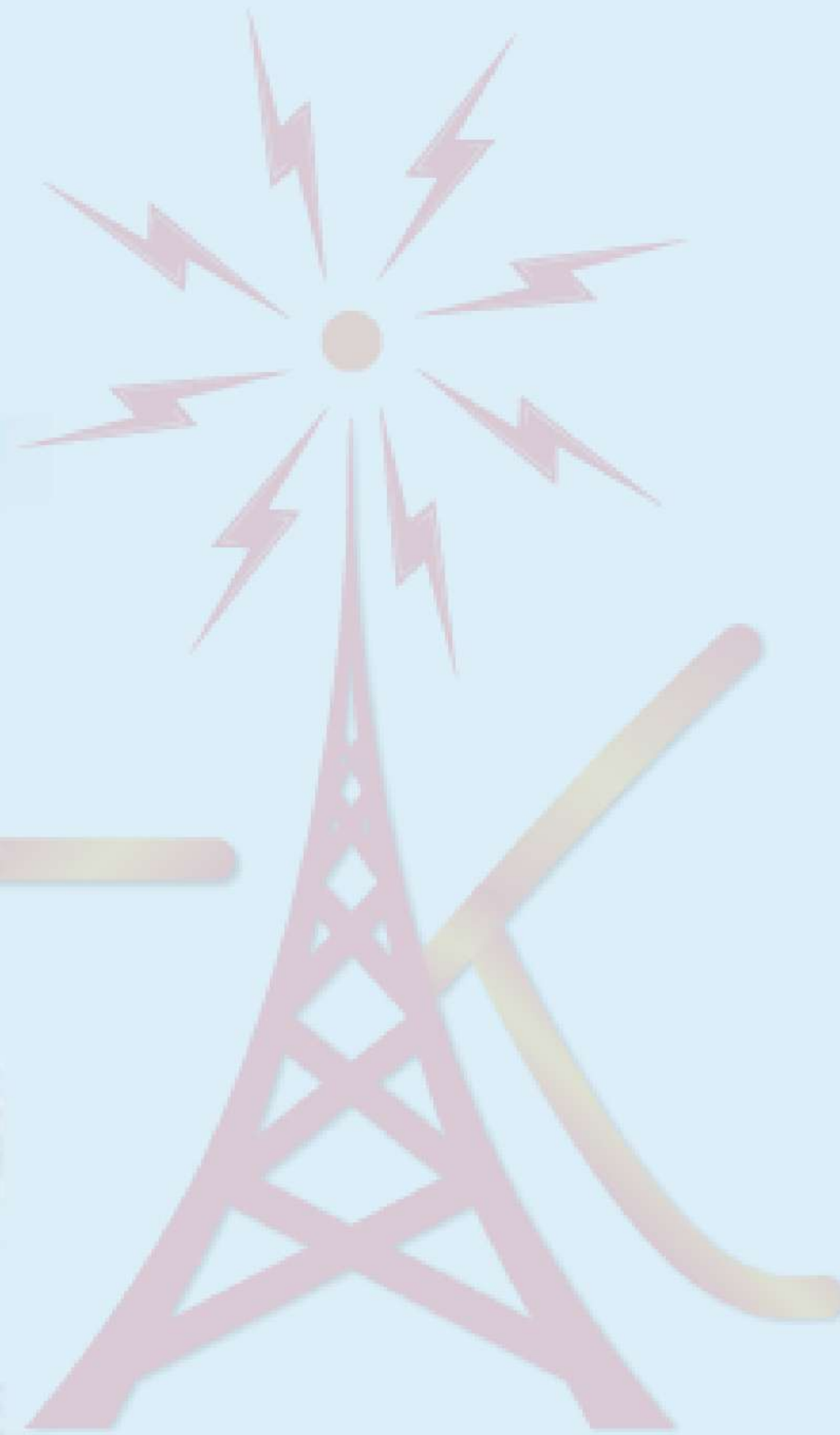- ☐ a. reverse biased
- ☐ b. neutral biased
- ☐ c. forward biased
- ☐ d. floating biased



approximate output waveform
in fig. 1, select the correct circuit
in fig.2 that will give this
approximate output waveform?

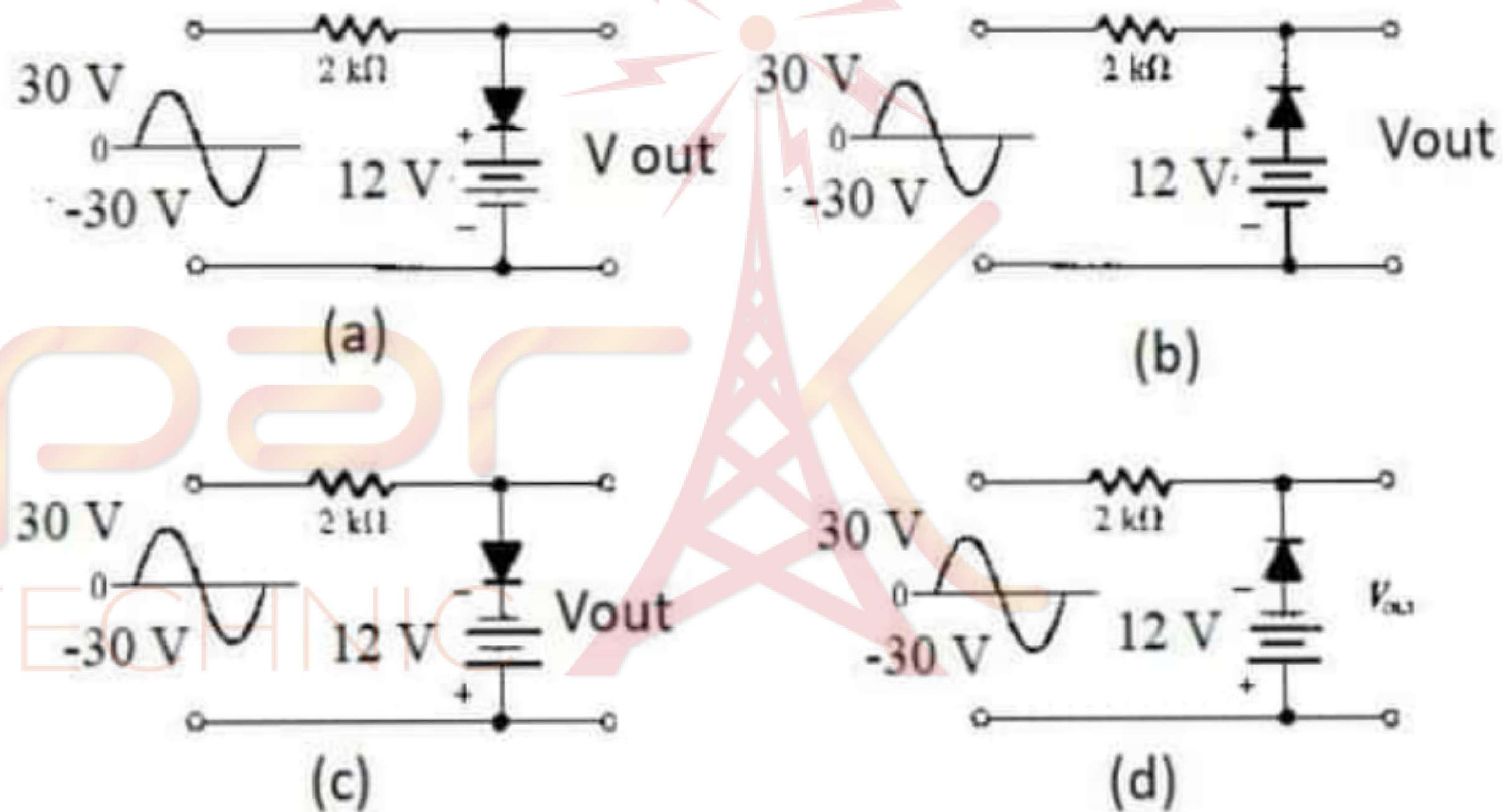


Fig. 2