

ELECTRICAL CIRCUITS LAB-5

Question 25

Not yet answered

Marked out of 2.00

 Flag question

Voltmeter on series will act as

Select one:

- ☐ A. Short circuit
- ☒ B. Open circuit

ELECTRICAL CIRCUITS LAB-5

Question 22

Not yet answered

Marked out of 2.00

Flag question

Mesh analysis is a method depends on:

Select one:

- ☒ A. Kirchhoff's voltage law (KVL)
- ☐ B. ohm's law
- ☐ C. Kirchhoff's current law (KCL)

ELECTRICAL CIRCUITS LAB-5

Question 18

Not yet answered

Marked out of 2.00

Flag question

An ideal ammeter has equivalent resistance =

Select one:

- ☐ A. R Load
- ☐ B. Infinity
- ☒ C. Zero

ELECTRICAL CIRCUITS LAB-5

Question 19

Not yet answered

Marked out of 2.00

Flag question

Nodal analysis is a method depends on


Select one:

- ☒ A. Kirchhoff's current law (KCL)
- ☐ B. ohm's law
- ☐ C. Kirchhoff's voltage law (KVL)



ELECTRICAL CIRCUITS LAB-5

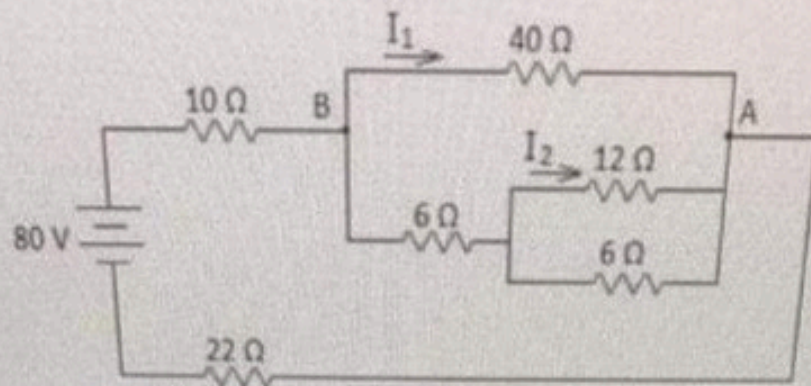The equivalent resistance seen by the source (R_{eq}) is:



Select one:

- ☐ A. 8 Ω
- ☐ B. 18 Ω
- ☐ C. 26 Ω
- ☒ D. 40 Ω

CTRICAL CIRCUITS LAB-5

16


answered

out of 2.00

g question

superposition

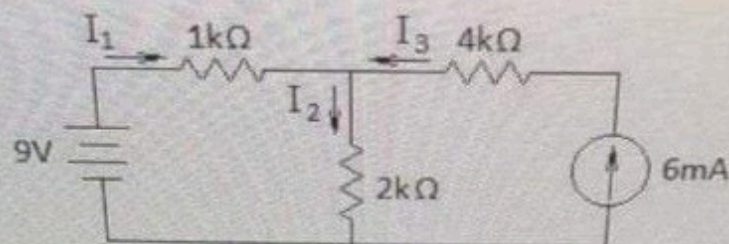The current I_2 due to the current source only is




Select one:

- ☐ A. 4 mA
- ☒ B. 2 mA
- ☐ C. 6 mA
- ☐ D. 8 mA

TRICAL CIRCUITS LAB-5

superposition

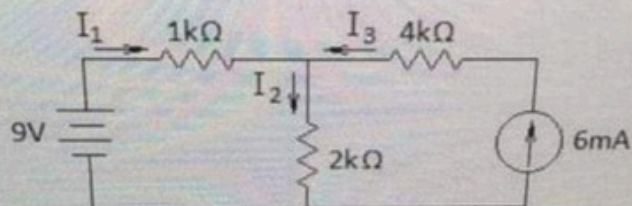The current I_2 due to the voltage source only is



Select one:

- ☐ a. 6 mA
- ☐ b. 9 mA
- ☒ c. 3 mA
- ☐ d. 4.5 mA

ELECTRICAL CIRCUITS LAB-5

Above the resonant frequency, the load will become:..

Select one:

- ☐ A. Capacitive
- ☐ B. Resistive
- ☒ C. Inductive


14

answered

d out of 2.00

ag question

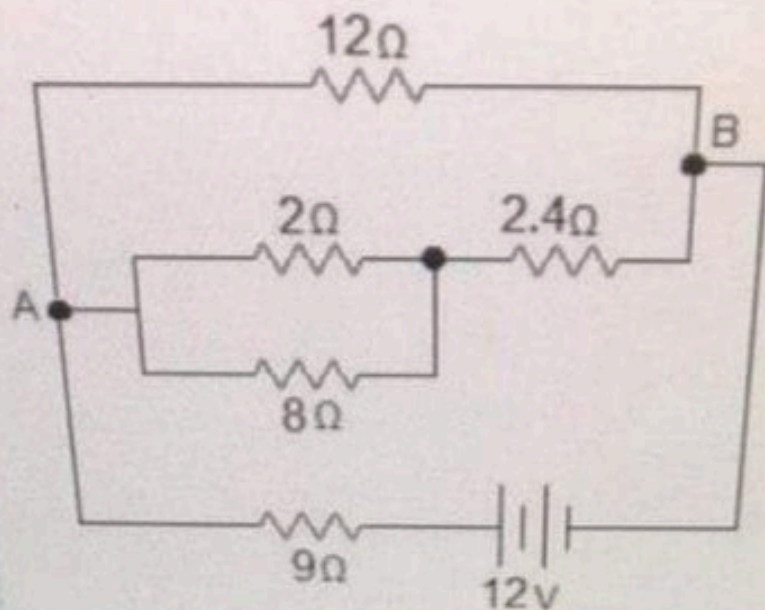The equivalent resistance seen by the source (R_{eq}) is:



Select one:

- ☒ A. 12 Ω
- ☐ B. 15 Ω
- ☐ C. 3 Ω
- ☐ D. 9 Ω

ELECTRICAL CIRCUITS LAB-5

Question 11

Not yet answered

Marked out of 2.00

Flag question

يتم توصيل الفولتميتر على

Select one:

☐ A. التوالي

☒ B. بالتوازي

ELECTRICAL CIRCUITS LAB-5

يقرأ الفولتميتر الجهد بصيغة

Select one:

- ☐ A. Transient voltage
- ☐ B. Peak voltage
- ☒ C. RMS voltage

RICAL CIRCUITS LAB-5

A capacitor and a resistor are connected in series to a sine wave generator. The frequency is set so that the capacitive reactance is equal to the resistance and thus, an equal amount of voltage appears across each component. If the frequency was decreased

Select one:

- ☒ A. $V_C > V_R$
- ☐ B. $V_R > V_C$
- ☐ C. $V_C = V_R$

Next page

RICAL CIRCUITS LAB-5

The reactance (X) of an inductor of 15 mH at a frequency of 60 Hz is

Select one:

- ☐ A. 0.17 K Ω
- ☐ B. 0.17 Ω
- ☐ C. 5.65 K Ω
- ☒ D. 5.65 Ω

ELECTRICAL CIRCUITS LAB-5

Question 3

Not answered

Time left out of 2.00

Flag question


Which of the following combinations of components represents an impedance of $110 + j 314 \Omega$ at a frequency of 100 Hz

Select one:

- ☐ A. An inductor of 50 mH in series with a capacitor of 5 μF
- ☒ B. A resistor of 110 Ω in series with an inductor of 500 mH
- ☐ C. A resistor of 110 Ω in series with a capacitor of 5 μF
- ☐ D. A resistor of 314 Ω in series with an inductor of 5 mH

Next page

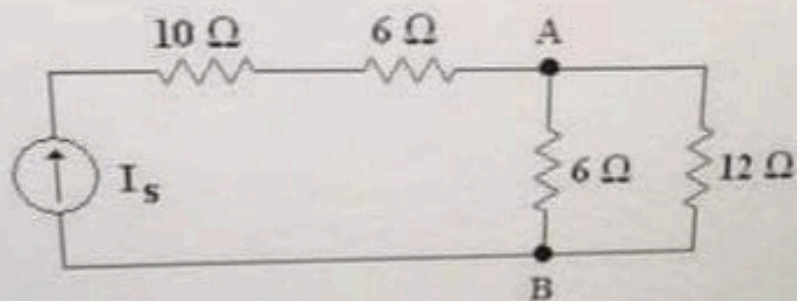The equivalent resistance seen by the source (R_{eq}) is:



Select one:

- ☐ A. $12\ \Omega$
- ☒ B. $20\ \Omega$
- ☐ C. $4\ \Omega$
- ☐ D. $22\ \Omega$

يتم توصيل الأميتر على

Select one:

☒ A. التوالي

☐ B. التوازي