


Question 3

Not yet answered

Marked out of 2.00

Flag question

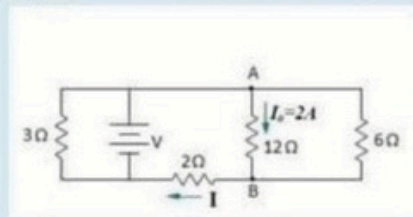Calculate the equivalent resistance of this circuit



Select one:

- ☐ A. 9Ω
- ☐ B. 7.2Ω
- ☐ C. 3.4Ω
- ☒ D. 2Ω

Next page

Question 4

Not yet answered

Marked out of 2.00

Flag question

If one of the resistors in a parallel circuit was removed, the total resistance

Select one:

- ☐ A. Remains the same
- ☒ B. Increases
- ☐ C. Decreases by the value of the removed resistor

Next page

QUIZ NAVIGATION

1	2	3	4	5	6	7	8
9	10	11	12	13	14	15	16
17	18	19	20	21	22	23	24

30104214- ELECTRICAL CIRCUITS LAB-6

Question 2

Not yet answered

Marked out of 2.00

Flag question

عند تردد الرنين في دائرة على التوالي يكون

Select one:

- ☒ A. كل الاجابات صحيحة
- ☐ B. التيار اعلى ما يمكن
- ☐ C. المقاومة اقل ما يمكن
- ☐ D. الجهد على المواسع مساوي للجهد على الملف

Next page

QUIZ NAVIGATION

30104214

ELECTRICAL CIRCUITS LAB-6

Question 1

Not yet answered

Marked out of 2.00

Flag question

في واحدة من طرق التحليل التالية يتم تبسيط الدارة المعقدة متعددة المصادر الى مجموعة دارات بسيطة لكل دائرة مصدر واحد فقط

Select one:

- ☐ A. nodal analysis
- ☐ B. mesh analysis
- ☒ C. superposition method
- ☐ D. thevenin

Next page

QUIZ NAVIGATION



ELECTRICAL CIRCUITS LAB-1

ELECTRICAL CIRCUITS LAB-1 > 24 July - 30 July > الامتحان القصير

The Thevenin equivalent voltage for a given circuit, found by

Select one:

- ☒ A. Opening the output terminals
- ☐ B. Shorting the output terminals
- ☐ C. Opening the voltage source
- ☐ D. Shorting the voltage source

ELECTRICAL CIRCUITS LAB-1

ELECTRICAL CIRCUITS LAB-1 » 24 July - 30 July » الامتحان النهائي

In the parallel connection:

Select one:

- ☐ A. The equivalent resistance equals the summation of the resistances included in the circuit.
- ☐ B. The currents applied on all the resistors are the same
- ☒ C. The voltages applied on all the resistors are the same
- ☐ D. All the answers are right


RICAL CIRCUITS LAB-1

CIRCUITS LAB-1 > 24 July - 30 July > الامتحان الصفي

In the series connection:

Select one:

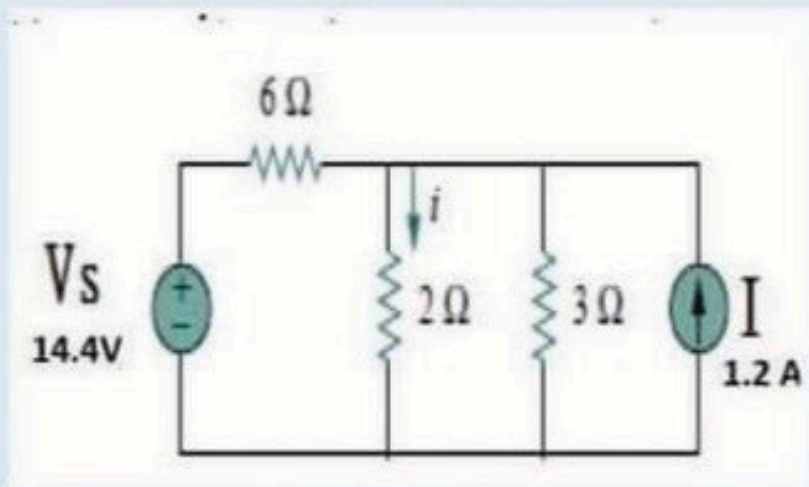- ☐ A. The current flowing in the circuit is constant along the circuit
- ☐ B. The voltage of the source equals the summation of the voltages on the included resistors in the circuit
- ☒ C. All the answers are right
- ☐ D. The equivalent resistance equals the summation of the resistances included in the circuit



The current i due to voltage source only is: (superposition)

Select one:

- ☐ A. 0.8 A
- ☒ B. 1.2 A
- ☐ C. 1.6 A
- ☐ D. 2 A

ELECTRICAL CIRCUITS LAB-2

Below the resonant frequency, the load will become

Select one:

- ☐ A. Resistive
- ☐ B. Inductive
- ☒ C. Capacitive

04214-ELECTRICAL CIRCUITS LAB-1

04214-ELECTRICAL CIRCUITS LAB-1 ➤ 24 July - 30 July ➤ الامتحان التصفي

Question 12

Not yet answered

Marked out of 2.00

🚩 Flag question

The unit of resistance is:

Select one:

- ☐ A. Volt
- ☒ B. Ohm
- ☐ C. Ampere

Question 11

Not yet answered

Marked out of 2.00

Flag question

The Thevenin equivalent voltage for a given circuit, found by

Select one:

- ☒ A. Opening the output terminals
- ☐ B. Shorting the output terminals
- ☐ C. Opening the voltage source
- ☐ D. Shorting the voltage source

Question 10

Not yet answered

Marked out of 2.00

 Flag question

Where current division occurs?

Select one:

- ☐ A. Series connected resistors
- ☐ B. Both series and parallel resistors
- ☒ C. Parallel connected resistors
- ☐ D. When resistors are equal

Next

The resistance is measured by:

Select one:

- ☐ A. Ammeter
- ☒ B. Ohmmeter
- ☐ C. Voltmeter

ON

4	5	6	7
11	12	13	14

Question 6

Not yet answered

Marked out of 2.00

Flag question

Voltmeter is connected in:

Select one:

- ☒ A. Parallel
- ☐ B. Series

Question 8

Not yet answered

Marked out of 2.00

Flag question

Where voltage division occurs?

Select one:

- ☐ A. When resistors are equal
- ☐ B. Parallel connected resistors
- ☐ C. Both series and parallel resistors
- ☒ D. Series connected resistors

Question 5

Not yet answered

Marked out of 2.00

Flag question

In the parallel connection:

Select one:

- ☐ A. The equivalent resistance equals the summation of the resistances included in the circuit.
- ☐ B. The currents applied on all the resistors are the same
- ☒ C. The voltages applied on all the resistors are the same
- ☐ D. All the answers are right

5	6	7
12	13	14

Question 4

Not yet answered

Marked out of 2.00

Flag question

Mesh current method is a method based on:

Select one:

- ☒ A. Kirchhoff Voltage Law
- ☐ B. Kirchhoff Current Law

6	7
13	14

Question 3

Not yet answered

Marked out of 2.00

Flag question

In a network, maximum power transfer occurs when

Select one:

- ☐ A. $R_{\text{thevenin}} + R_{\text{load}} = 1$
- ☐ B. $R_{\text{thevenin}} / R_{\text{load}} = 0$
- ☒ C. $R_{\text{thevenin}} = R_{\text{Load}}$

214-ELECTRICAL CIRCUITS LAB-1

3-30104214-ELECTRICAL CIRCUITS LAB-1 ▶ 24 July - 30 July ▶ الامتحان التصفي

Question 1

Not yet answered

Marked out of 2.00

Flag question


In superposition method

Select one:

- ☐ A. Voltage source become open circuit, and current source become short circuit
- ☐ B. Both Voltage source and current source become short circuit
- ☐ C. Both Voltage source and current source become open circuit
- ☒ D. Voltage source become short circuit, and current source become open circuit

wered
of 2.00
ation

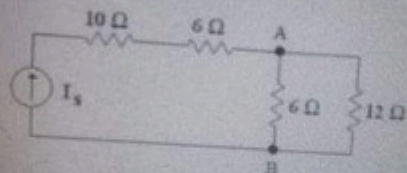
If $V_{AB} = 32\text{V}$, the source current is:



Select one

- ☐ A. 4 A
- ☐ B. 5.33 A
- ☐ C. 2.67 A
- ☒ D. 8 A

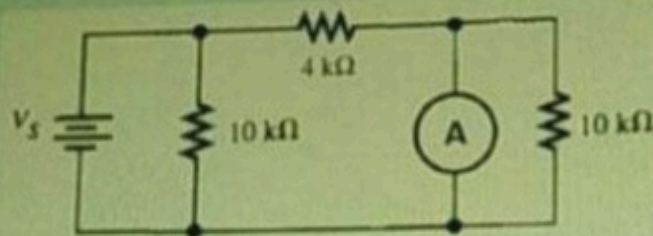For the circuit shown when $V_s = 12\text{V}$, then the ammeter reading (mA) is



Select one:

☐ A. 1.5 mA

☒ B. 3 mA

☐ C. 2.5 mA

☐ D. 2 mA

الجواب الصحيح →